

# Mercurial Machine Filter

Guy John  
`guy@rumblesan.com`

May 13, 2023

## 1 Introduction

Analysis of the Mercurial Machine filter. Heavily based on the Serge VCFQ, but also with influence from the Mutable Instruments Blades. Much of this is pulled verbatim from the SSM2164 SVF Analysis by Emilie Gillet and then just somewhat modified.

## 1.1 Notations

$R_i$  is the value of the resistor through which the input signal is fed to the circuit.

$R_g$  is the value of the resistor through which the HP and LP outputs are fed back into the input.

$R_q$  is the value of the resistor through which the attenuated BP output is fed back into the input.

$R$  and  $R_s$  are the values of the resistor at the voltage divider input of the OTAs.

$R_f$  is the value of the resistor through which the current at the output of the Q attenuator is converted back into a voltage.

$C$  is the value of the integrators' capacitors.

$v_{cv}$  is the cutoff frequency control voltage.

$v_q$  is the resonance control voltage.


$v_i(s)$  is the input voltage.

$v_{hp}(s)$ ,  $v_{bp}(s)$  and  $v_{lp}(s)$  are the high-pass, band-pass and low-pass output voltages.

For reference, the standard second-order filter transfer functions are:

$$\begin{aligned} H_{lp}(s) &= \frac{1}{s^2T^2 + \frac{1}{q}sT + 1} \\ H_{bp}(s) &= \frac{1}{\frac{q}{sT} + qsT + 1} \\ H_{hp}(s) &= \frac{1}{\frac{1}{s^2T^2} + \frac{1}{qsT} + 1} \end{aligned}$$

## 1.2 OTA Integrator Cell

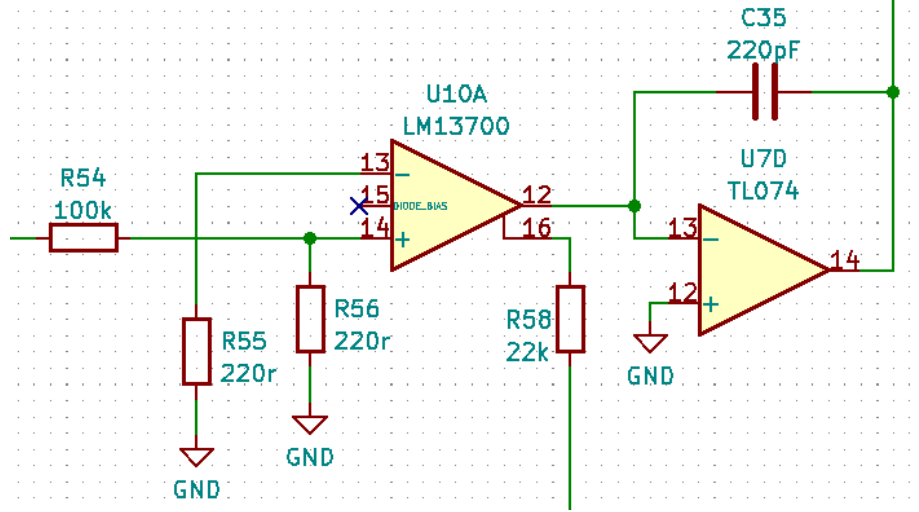

The transfer function of an OTA is:

$$i_o = g_m(v_+ - v_-)$$

$$i_o = 19.2i_{cv}(v_+ - v_-)$$

If  $R_f$  is equal to  $R_i$  Kirchoff in  $v_+$  gives:

$$\frac{1}{R}(v_i(s) - v_+(s)) = \frac{1}{R_s}v_+(s)$$

$$R_s v_i(s) - R_s v_+(s) = R v_+(s)$$

$$R_s v_i(s) = R v_+(s) + R_s v_+(s)$$

$$R_s v_i(s) = v_+(s)(R + R_s)$$

$$v_+(s)(R + R_s) = R_s v_i(s)$$

$$v_+(s) = \frac{R_s}{R + R_s}v_i(s)$$

The current  $i_c$  at the output if the OTA is:

$$i_c(s) = g_m(v_+(s) - v_-(s))$$

$$= 19.2i_{cv}\left(\frac{R_s}{R + 2R_s}v_i(s) - 0\right)$$

$$= 19.2i_{cv}\frac{R_s}{R + 2R_s}v_i(s)$$

The voltage out of the OpAmp:

$$v_o(s) = \frac{-i_c(s)}{Cs}$$


$$v_o(s) = -19.2i_{cv} \frac{R_s}{Cs(R + 2R_s)} v_i(s)$$

So the transfer function is:

$$\alpha(s) = -19.2i_{cv} \frac{R_s}{Cs(R + 2R_s)} \quad (1)$$

### 1.3 Feedback Control

The gain of the feedback circuit is:

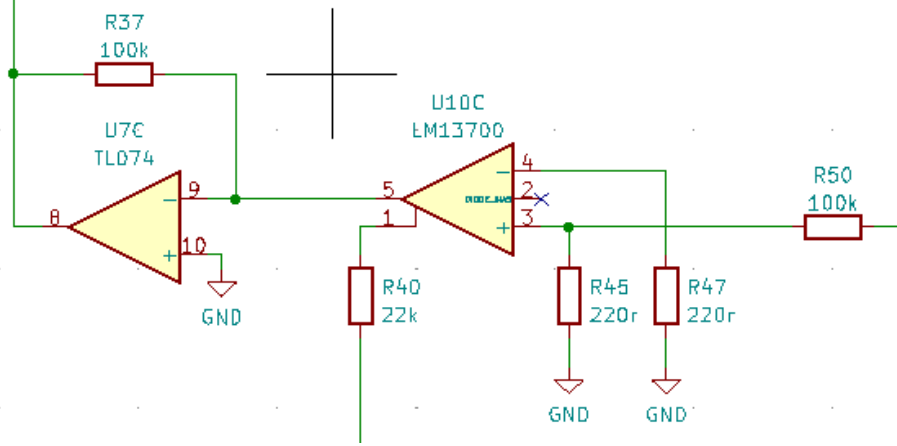

$$v_+ = v_i \frac{R_s}{R + R_s}$$

$$i_o = 19.2i_q(v_+ - v_-)$$

$$i_o = 19.2i_q(v_+ - 0)$$

$$i_o = 19.2i_q v_i \frac{R_s}{R + R_s}$$

$$i_o = R_f(v_- - v_o)$$

$$i_o = -R_f v_o$$

$$-R_f v_o = 19.2i_q v_i \frac{R_s}{R + R_s}$$

$$-R_f v_o = 19.2i_q v_i \frac{R_s}{R + R_s}$$

$$v_o = -19.2i_q v_i \frac{R_f R_s}{R_i + R_s}$$

$$\beta = -19.2i_q \frac{R_f R_s}{R_i + R_s}$$

## 1.4 Filter

$$\begin{aligned}\frac{v_i - v_-}{R_i} + \frac{v_{hp} - v_-}{R_g} + \frac{v_{lp} - v_-}{R_g} + \frac{v_{bp}\beta - v_-}{R_q} &= i_- = 0 \\ \frac{v_i}{R_i} + \frac{v_{hp}}{R_g} + \frac{v_{lp}}{R_g} + \frac{v_{bp}\beta}{R_q} &= 0\end{aligned}$$

It is important to note that  $v_{bp}(s) = v_{hp}(s)\alpha(s)$ , and  $v_{lp}(s) = v_{hp}(s)\alpha(s^2)$ .

### 1.4.1 High-pass

$$\begin{aligned}\frac{v_{hp}(s)}{R_g} &= -\frac{v_i(s)}{R_i} - \frac{v_{lp}(s)}{R_g} - \frac{v_{bp}(s)\beta}{R_q} \\ \frac{v_{hp}(s)}{R_g} &= -\frac{v_i(s)}{R_i} - \frac{v_{hp}(s)\alpha(s^2)}{R_g} - \frac{v_{hp}(s)\alpha(s)\beta}{R_q} \\ \frac{v_i(s)}{R_i} &= -\frac{v_{hp}(s)}{R_g} - \frac{v_{hp}(s)\alpha(s^2)}{R_g} - \frac{v_{hp}(s)\alpha(s)\beta}{R_q} \\ H_{hp}(s) &= \frac{v_{hp}(s)}{v_i(s)} \\ \frac{v_i(s)}{R_i} &= -v_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\ \frac{1}{R_i} &= -H_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\ \frac{-1}{R_i} &= H_{hp}(s)\left(\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}\right) \\ H_{hp}(s) &= \frac{-1/R_i}{\frac{1}{R_g} + \frac{\alpha(s^2)}{R_g} + \frac{\alpha(s)\beta}{R_q}} \\ &= \frac{-R_g/R_i}{1 + \frac{R_g\alpha(s)\beta}{R_q} + \alpha(s^2)}\end{aligned}$$

### 1.4.2 Low-Pass

$$\begin{aligned}
H_{lp}(s) &= \frac{v_{lp}(s)}{v_i(s)} \\
&= \frac{v_{hp}(s)}{v_i(s)} \alpha^2(s) \\
&= \frac{-R_g/R_i}{\frac{1}{\alpha^2(s)} + \frac{R_g\beta}{R_q\alpha(s)} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{\alpha^2(s)} + \beta \frac{R_g}{R_q} \frac{1}{\alpha(s)} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{(-19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + (-19.2i_q \frac{R_f R_s}{R_i + R_s}) \frac{R_g}{R_q} \frac{1}{-19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{(19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{1}{19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{1}{\frac{1}{s^2} (19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{1}{19.2i_{cv} \frac{1}{s} \frac{R_s}{Cs(R+2R_s)}} + 1} \\
&= \frac{-R_g/R_i}{\frac{s^2}{(19.2i_{cv} \frac{R_s}{Cs(R+2R_s)})^2} + 19.2i_q \frac{R_f R_s}{R_i + R_s} \frac{R_g}{R_q} \frac{s}{19.2i_{cv} \frac{R_s}{Cs(R+2R_s)}} + 1}
\end{aligned}$$

One simplification worth making is to say that  $R_q = R_g$ .

By comparing with the standard form of a second order filter transfer function we can work out the following.

Pass-band gain,  $-\frac{R_g}{R_i}$

Cutoff frequency,  $19.2i_{cv} \frac{R_s}{C2\pi(R+2R_s)}$

Quality factor,  $\frac{1}{19.2i_q \frac{R_f R_s}{R_i + R_s}}$

### 1.5 Calculating cutoff frequencies

Given the calculation for frequency, and picking some standard values we can calculate cutoff for different  $i_{cv}$  values.

$R$  is 100k

$R_s$  is 220r

$C$  is 220pF

$$f = 19.2i_{cv} \frac{220}{220 * 10^{-12} * 2\pi(100000 + 2(220))} \quad (2)$$

for  $i_{cv}$  of 0.5ma  $f = 15212Hz$

for  $i_{cv}$  of 0.3ma  $f = 9127Hz$

for  $i_{cv}$  of 0.1ma  $f = 3042Hz$

for  $i_{cv}$  of 0.05ma  $f = 1521Hz$

for  $i_{cv}$  of 0.01ma  $f = 304Hz$

## 1.6 Calculating resonance

A quality factor of 1/2 gives no resonance, whilst the resonance (and likelihood of self oscillating) increases as Q goes to infinity.

$R_f$  is 100k

$R_i$  is 100k

$R_s$  is 220r

$C$  is 220pF

$$q = \frac{1}{19.2i_q \frac{100000*220}{100000+220}} \quad (3)$$

for  $i_q$  of 0.5ma  $q = 0.47$

for  $i_q$  of 0.3ma  $q = 0.79$

for  $i_q$  of 0.1ma  $q = 2.37$

for  $i_q$  of 0.05ma  $q = 4.75$

for  $i_q$  of 0.01ma  $q = 23.7$